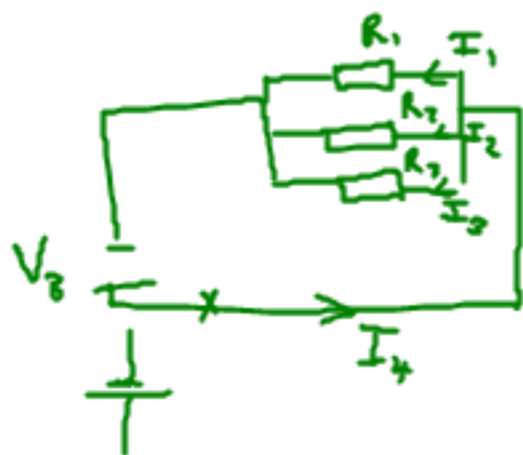


8)




$$I_4 = I_1 + I_2 + I_3$$

$$-R_3 I_3 + V_B = 0 \quad I_3 =$$

$$-R_2 I_2 + V_B = 0 \quad I_2 =$$

$$-R_1 I_1 + V_B = 0 \quad I_1 =$$


$$c) \quad P = \dot{W} \\ P = I^2 R$$

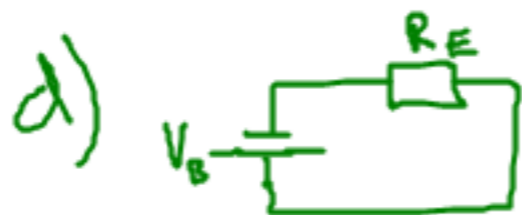

$$\frac{1}{R_E} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$P = \frac{V^2}{R}$$

10

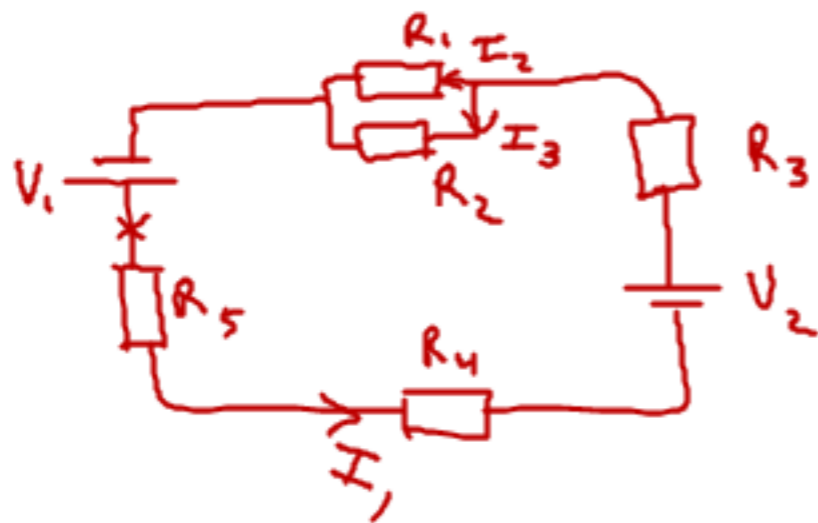

$$I_1 = I_2 + I_3$$

$$-R_5 I_1 - R_4 I_1 + V_2 - R_3 I_1 - R_1 I_2 + V_1 = 0$$


$$-R_5 I_1 - R_4 I_1 + V_2 - R_3 I_1 - R_2 I_3 + V_1 = 0$$

$$-R_1 I_2 + R_2 I_3 = 0$$

b)  $P = I^2 R$

12)

$$R = .037 \Omega$$

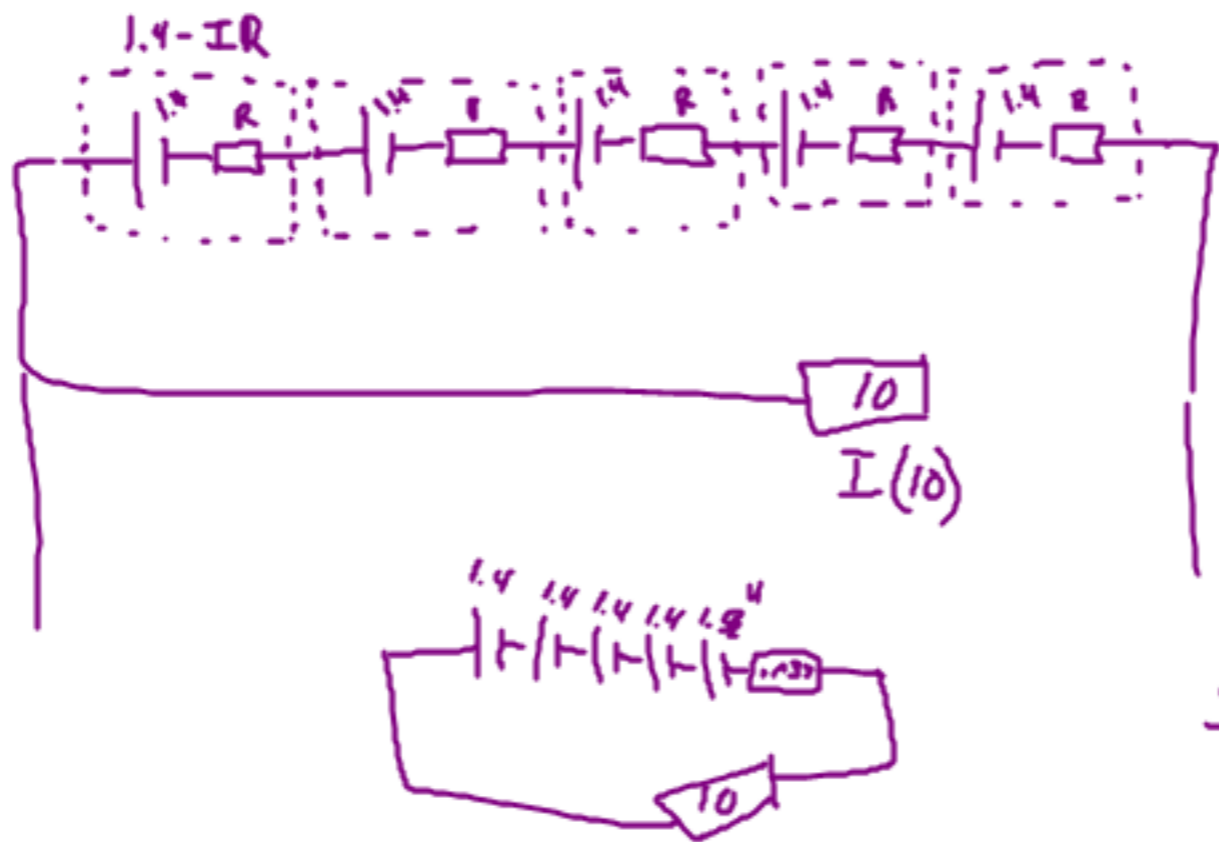

$$5(1.4 - I(.037)) - V = 10I$$

$$(1.4 - I(.037)) = 2I$$

$$1.4 = I(2.037)$$


$$5(1.4) - I(.037) = 10I$$

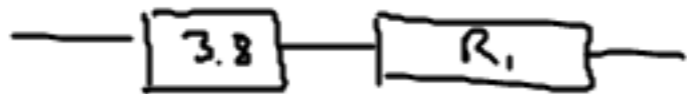14)



$$R_E = 8.6 \Omega$$

$$\frac{1}{R_1} = \frac{1}{7.9} + \frac{1}{R}$$



$$R_E = 3.8 + R_1$$

